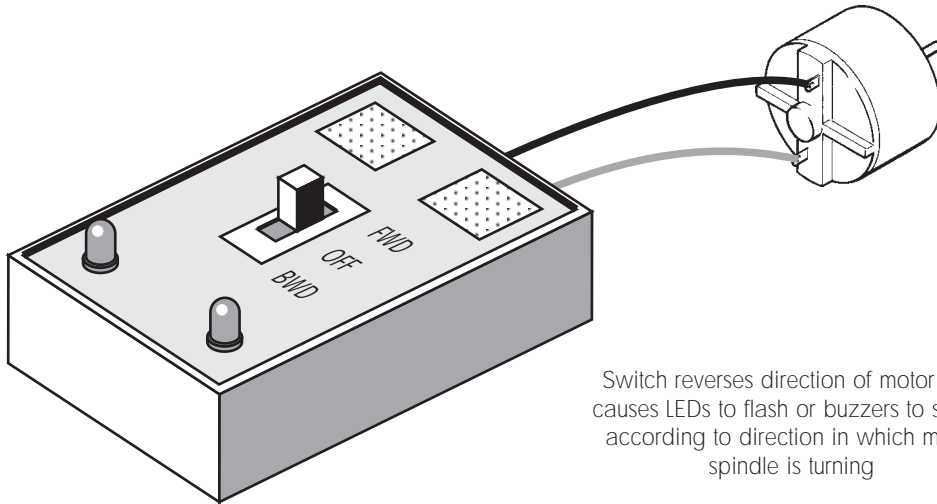


CONTROLLER FOR ANIMATRONIC TOY

Source: John Kelly Boys' Technology College



Switch reverses direction of motor and causes LEDs to flash or buzzers to sound according to direction in which motor spindle is turning

